

# Indian Institute of Information Technology, Allahabad

Project B.Tech E.C.E 5<sup>th</sup> Semester

## *Secure UART Implementation on FPGA*

Project Supervisor : Dr. Sunny Sharma

---


Group Members: IEC2014002 Ritwick Sundar  
IEC2014090 Utkarsh Singh  
IEC2014097 Kshitij Garg

# Abstract


- UART - Universal Asynchronous Transmitter Receiver is a computer hardware device for asynchronous communication in conjunction with communication standards like RS-232.
  - UART works on a serial-to-parallel and parallel-to-serial data transfer protocol.
  - Mostly used for short-distance, low-cost data exchange between computer and peripherals.
- 
- Secure UART - Data transfer is secured using Secure Hashing Algorithm-1 (SHA-1) mainly for high speed integrity checks with end-to-end control in industrial uses.
  - SHA-1 : It is a cryptographic hash function designed by the United States National Security Agency and is a U.S. Federal Information Processing Standard published by the United States NIST.
  - SHA-1 produces a 40 digit hex hash value known as a message digest.

# Block Diagram


## Full UART

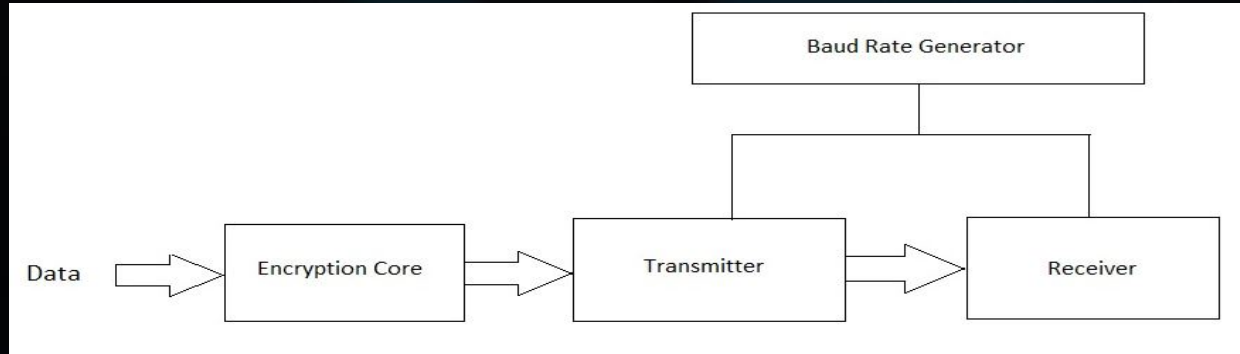

## Transmitted Bitstream

 
 
### Functional Block Diagram of the Baud Rate Generator



#### Input Ports

clk: Input system clock to the Baud Rate Generator


rst: Input reset that resets the Transmitter

#### Output Ports

txclk: Output of the Baud Rate Generator that acts as Input clock to the Transmitter. Transmission and Reception will occur when the system clock to both the Transmitter and Receiver are synchronised.

rxclk: Output of the Baud Rate Generator that acts as Input clock to the Receiver.
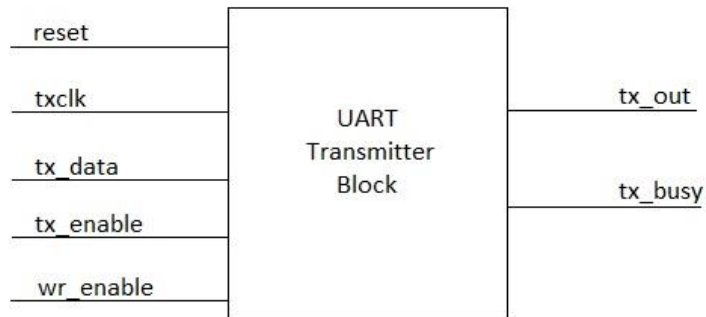
## Functional Block Diagram of UART Transmitter



### Input Ports:

reset: Resets the clock  
txclk: Input clock to the Transmitter  
tx\_data: 8 bit data to be transmitter by the Transmitter  
tx\_enable: Output of the Baud Rate Generator which tells whether transmitter should transmit data or not  
wr\_enable: Write enable

### Output Ports:

tx\_out : Output of the Transmitter that transmits the data stream to the Receiver.  
tx\_busy: If the Transmitter is in the IDLE state, the tx\_busy goes low and Transmitter is free to transmit to the Receiver. If not in IDLE state, tx\_busy stays high.

# Introduction

UART (Universal Asynchronous Receiver Transmitter) is an integrated circuit, which is used for transmitting and receiving data asynchronously via the serial port on the computer. It contains a parallel-to-serial converter for data transmitted from the computer and a serial-to-parallel converter for data coming in via the serial line. The UART also has a buffer for temporarily storing data from high-speed transmissions.

UART will usually provide additional circuits for signals that can be used to indicate the state of the transmission media and to regulate the flow of data in the event that the remote device is not prepared to accept more data.

The typical UART consists of three basic modules :

- Baud Rate Generator
- Transmitter
- Receiver

# Secure UART

- The transmitted data from a UART is not secured by the UART module itself but by the software of the electronic device the UART is connected to.
- In this project we aim to integrate both the Encryption module and UART together for a full Hardware implementation and create a Secure UART.
- The messages can be encoded in different protocols like AES ,Tiny Encryption, etc based on specific requirements.
- For our project we aim to implement Secure Hashing Algorithm - 1 (SHA-1) with the UART module.
- Hence our transmitted messages will be a 40 digit hex code in the final implementation.

# Advantages of Hardware Implementation

- The hardware based encryption uses a device's on-board security to perform encryption and decryption.
- It is self-contained and does not require the help of any additional software or driver.
- Free from any possibility of contamination, malicious code infection, or vulnerability.
- Minimum user interaction and does not cause performance degradation.
- Hardware Implementation offers stronger resilience against brute force attacks.
- Faster than any software implementation.
- Reduces CPU overhead as the hardware itself is responsible for Encryption.



## **Progress So-Far**

- Learnt Basics of Verilog HDL
- Completed Baud Rate Generator Module
- Completed Transmitter Module
- Simulated Transmitter to transmit an 8 bit code on Xilinx Vivado 2016.2
- Timing Analysis of the modules

## **Deliverables till End-Sem**


- Full UART Module (Baud Rate Generator, Transmitter, Receiver)
- SHA-1 Encryption Core
- Integrating SHA-1 Core with UART
- Full Timing and Performance Analysis
- FPGA Implementation

# Baud Rate Generator

- The Baud Rate Generator contains 2 internal counters - one for Transmitter and one for Receiver clock.
- The Counters are used as Frequency Dividers.
- The Receiver clock frequency is normally 16 times the Transmitter clock frequency for oversampling.
- The Baud Rate Generator implemented uses Divide by 16 to create the 16:1 receiver to transmitter clock speed ratio.
- The Divide by 16 counter is a 4 bit counter. Once the counter reaches 15 , the transmitter clock goes high and counter is reset to 0.
 
# Timing Diagram

- Timing Diagram of Transmitter clock ( System Clock / 16 ) as generated by Baud Rate Generator.



# Transmitter

The Transmitter takes in input from an 8 bit register and waits for wr\_enable ( CPU signal ) to transmit.

By convention the default output is kept high to signify that line is active but idle.

Its function is to convert the parallel data to serial format and transmit it,

An even parity module has been created to send along the data for integrity check.


Inputs to the Transmitter include : Reset, Tx\_Enable(Clock) ,Wr\_enable, Tx\_data and parity bit

Ouputs from the Transmitter include : Tx\_Out , Tx\_Busy flag.

# Transmitter

- The Transmitter has been implemented as a Finite State Machine with 5 States :
  1. IDLE - In Idle state the transmitter waits for the wr\_enable (The CPU signal that tells UART it is sending data to be transmitted).
  2. START- In Start state the transmitter makes the tx\_out low to signal the start of data transmission to the receiver and sends out a 0 bit.
  3. TX - The 8 bit data is now sent LSB first so that the data received by the receiver is in big-endian format (MSB-left LSB-right).
  4. PARITY –The transmitter calculates the even parity of the transmitted code and appends it after the data transmission ; hence taking 1 bit for parity.
  5. STOP - The Id\_tx\_data is made 0 and transmitter sends out 1 signalling completion of data transfer. The transmitter returns to IDLE state after STOP and waits for wr\_enable.


# Transmitter FSM

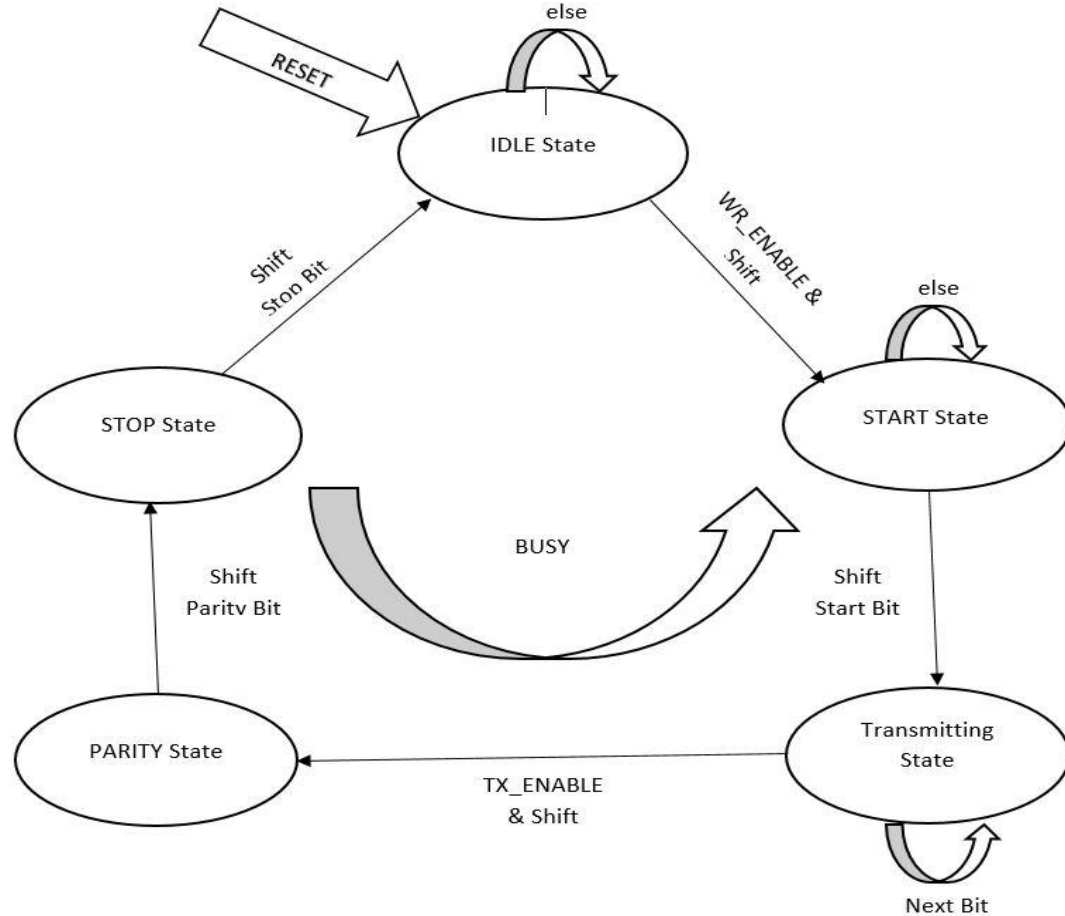

# Overall Timing Diagram



# RTL Synthesis

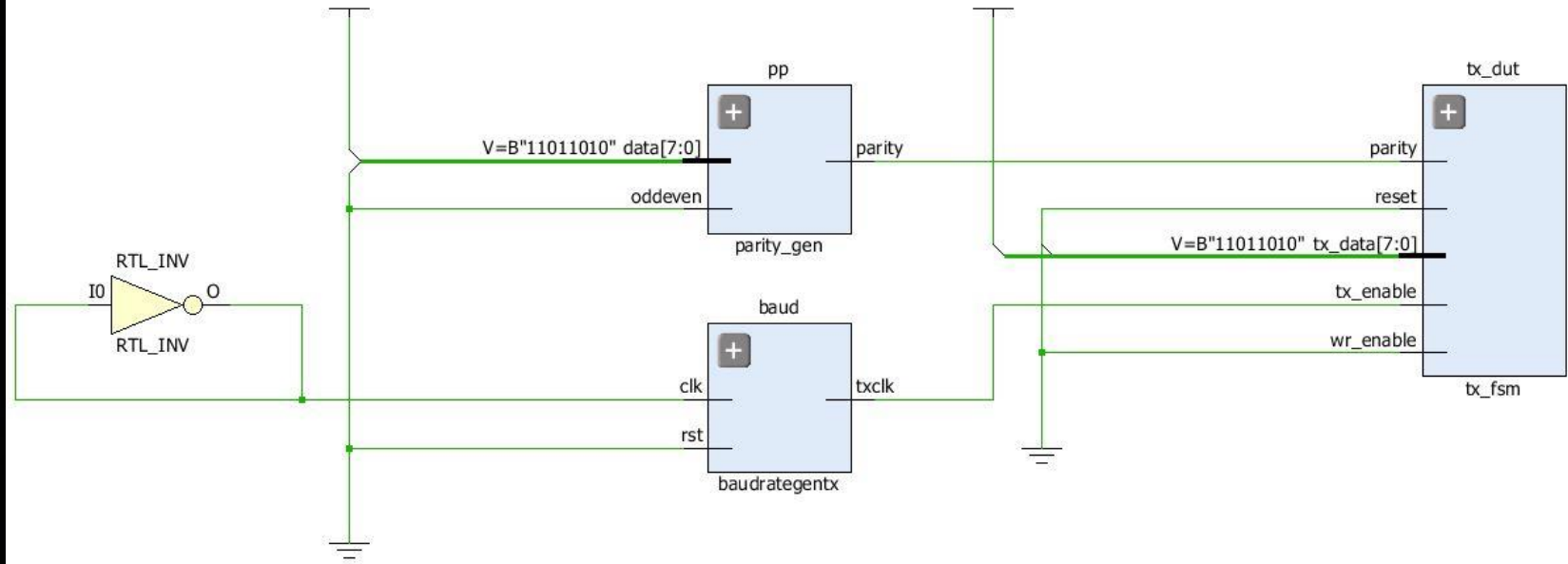



# Code : // Baud Rate Generator

#(parameter width = 4, N = 8)

```
module baudrategentx(clk, rst, txclk);
```

```
    input clk, rst;  
    output txclk;
```

```
    reg [width - 1:0] r_reg, txclk_track;  
    wire [width - 1:0] r_nxt;
```

```
    always @ (negedge clk or negedge rst) begin
```

```
        if (rst) begin
```

```
            r_reg <= 0;
```

```
            txclk_track <= 1'b0;
```

```
        end
```

```
        else if (r_nxt == N) begin
```

```
            r_reg <= 0;
```

```
            txclk_track <= ~txclk_track;
```

```
        end
```

```
        else
```

```
            r_reg <= r_nxt;
```

```
    end
```

```
    assign r_nxt = r_reg + 1;
```

```
    assign txclk = txclk_track;
```

```
endmodule
```

# Code : // Parity Module

```
`timescale 1ns / 1ps
```

```
module parity_gen (  
    data      ,  
    oddeven   ,  
    parity  
);
```

```
    input [7:0] data;  
    input oddeven;  
    output parity;
```

```
    assign parity = (^data) ^ oddeven;
```

```
endmodule
```

# Code : // Transmitter

```
module tx_fsm (
    reset      ,
    tx_data    ,
    wr_enable  ,
    tx_enable  ,
    parity     ,
    tx_out     ,
    tx_busy
);
// Port declarations
input  reset      ;
input [7:0] tx_data ;
input  tx_enable  ;
input  wr_enable  ;
input  parity     ;
output tx_out     ;
output tx_busy    ;

// Internal Variables
reg [7:0] tx_reg ;
reg [3:0] tx_cnt ;
reg  tx_out     ;
reg                      tx_busy    ;
reg  ld_tx_data ;
reg [SIZE-1:0] state;

parameter SIZE = 5;
parameter IDLE = 3'b000, START = 3'b001, TX = 3'b010, PARITY = 3'b011, STOP = 3'b100;
```

```

always @ (negedge tx_enable)
if (reset) begin
    tx_busy    <= 1;
    tx_reg     <= 0;
    tx_cnt     <= 0;
    ld_tx_data <= 0;
    tx_out     <= 1;
    state <= IDLE;

    end
else
    case(state)
        IDLE : if (wr_enable) begin
            tx_reg <= tx_data;
            ld_tx_data <= 1;
            state <= START;
            tx_cnt <= 0;
            end
        START : if (!tx_enable) begin
            tx_busy <= 0;
            $display("TX of data has been started");
            if(tx_cnt == 0) begin
                $display("Counter Value : %b",tx_cnt);
                tx_out <= 0;
                end
            state <= TX;
            tx_cnt <= tx_cnt + 1;
            end
        TX : if (!tx_enable) begin
            tx_out <= tx_reg[tx_cnt -1];
            $display("Counter Value: %b",tx_cnt);
            tx_cnt <= tx_cnt +1 ;
            if(tx_cnt == 8) begin
                state <= PARITY;
                end
            end
    endcase
end

```

```

PARITY: if(!tx_enable) begin
    tx_out <= parity;
    state <= STOP;
    $display("Parity Bit: %b",parity);
    end

STOP : if(!tx_enable) begin
    ld_tx_data <= 0;

    tx_out <= 1;
    tx_cnt <= 0;
    state <= #1 IDLE;

    tx_busy    <= 1;
    $display("Counter Value: %b",tx_cnt);
    $display("TX of data has been completed");

    end

default : state <= #1 IDLE;
endcase
endmodule

```

# References

1. Basu, Debjani, Dipak K. Koley, and Hafizur Rahman. "Implementation of AES algorithm in UART module for secured data transfer." In Advances in Computing and Communications (ICACC), 2012 International Conference on, pp. 142-145. IEEE, 2012.
2. Fang, Yi-yuan, and Xue-jun Chen. "Design and simulation of UART serial communication module based on VHDL." In Intelligent Systems and Applications (ISA), 2011 3rd International Workshop on, pp. 1-4. IEEE, 2011.
3. Solanki, Yogendra Singh. "Performance Based Design and Implementation of a SHA-1 Hash Module on FPGA."
4. Verilog HDL : A Guide To Digital Design And Synthesis (IEEE 1364-2001 Compliant) – by Samir Palnitkar